

## CAPACITORS

1. A parallel condenser is charged and is disconnected from the battery. If the plates of the capacitor are moved further apart by insulating handles
  - 1) The charge becomes zero
  - 2) Capacitance becomes infinite
  - 3) The charge and capacitance increase
  - 4) The voltage across the plates increases
2. Parallel plate capacitor with air as the medium has the capacitance  $10 \mu\text{F}$ . The area of the capacitor is divided into two equal halves and filled with two media, having the dielectric constant  $K_1 = 2$  and  $K_2 = 4$ . The capacitance of the system will now be
  - 1)  $10 \mu\text{F}$
  - 2)  $20 \mu\text{F}$
  - 3)  $30 \mu\text{F}$
  - 4)  $40 \mu\text{F}$
3. Resistors  $R_1$  and  $R_2$  and the capacitor  $C$  are connected to a battery of E.M.F.  $V$  volts, through the switches  $S_1$  and  $S_2$  as shown in the figure. The capacitor will get fully charged to  $V$  volts when
  - 1)  $S_1$  is open and  $S_2$  is closed
  - 2)  $S_2$  is open and  $S_1$  is closed
  - 3)  $S_1$  and  $S_2$  are both open
  - 4)  $S_1$  and  $S_2$  are both closed
4. The resultant capacitance between the point A and B in the given circuit is
  - 1)  $C$
  - 2)  $C/2$
  - 3)  $2C$
  - 4)  $3C$
5. The energy stored in a  $50 \mu\text{F}$  capacitor charged to  $6 \text{KV}$  is the same as that required to lift a  $24\text{kg}$  mass. What would be the greatest vertical height through the mass could be raised ?
  - 1)  $1.8\text{m}$
  - 2)  $3.6\text{m}$
  - 3)  $0.9\text{m}$
  - 4)  $7.2\text{m}$
6. A parallel plate capacitor is to be made by inserting one of the sheets of dielectric material include below, between and in contact with two plates of copper

	K	d[in m]
1) Teflon	2	0.4
2) Quartz	3	0.8
3) Glass	4	1.0
4) Mica	5	1.2
7. Calculate the effective capacitance between A and B if the capacitance of the capacitor is  $1 \mu\text{F}$ .
  - 1)  $\infty$
  - 2) Zero
  - 3)  $\mu\text{f}$
  - 4)  $8 \mu\text{f}$

8. The capacitance of a parallel plate capacitor is  $C_0$ . If a dielectric of relative permittivity  $\epsilon_r$  and thickness equal to one fourth the plate separation is introduced between the plates, then its capacitance becomes  $C$ . The value of  $C/C_0$  is

- 1)  $\frac{5\epsilon_r}{4\epsilon_r+1}$
- 2)  $\frac{4\epsilon_r}{3\epsilon_r+1}$
- 3)  $\frac{3\epsilon_r}{2\epsilon_r+1}$
- 4)  $\frac{2\epsilon_r}{\epsilon_r+1}$

9. Four conducting plates each of area  $A$  are placed equidistant from each other. The inner plates are connected electrically to point A and the outer plates are electrically connected to point B as shown. The effective capacitance of the system is

- 1)  $\epsilon_0 A/d$
- 2)  $2 \epsilon_0 A/d$
- 3)  $3 \epsilon_0 A/d$
- 4)  $4 \epsilon_0 A/d$

10. The effective capacitance between the points P and Q of the arrangement shown in the figure is

- 1)  $\frac{1}{2} \mu F$
- 2)  $1 \mu F$
- 3)  $2 \mu F$
- 4)  $1.33 \mu F$

11. In the accompanying circuit, if the point c is connected to the point a and the point d is connected to the point b, the effective capacitance between the points a and b is

- 1)  $20 \mu F$
- 2)  $60 \mu F$
- 3)  $80 \mu F$
- 4)  $120 \mu F$

12. A fully charged capacitor has a capacitance  $C$ . It is discharged through a small coil of resistance wire embedded in a thermally insulated block of specific heat capacity  $s$  and mass  $m$ . If the temperature of the block is raised by  $\Delta T$ , the potential difference  $V$  across the capacitance is

- 1)  $\sqrt{\frac{2mC\Delta T}{s}}$
- 2)  $\frac{mC\Delta T}{s}$
- 3)  $\sqrt{\frac{mC\Delta T}{c}}$
- 4)  $\sqrt{\frac{2ms\Delta T}{c}}$

13. A  $10 \mu F$  capacitor is charged to a potential difference of 50 V and is connected to another uncharged capacitor in parallel. Now the common potential difference becomes 20 volt. The capacitance of second capacitor is

- 1)  $10 \mu\text{F}$
- 2)  $20 \mu\text{F}$
- 3)  $30 \mu\text{F}$
- 4)  $15 \mu\text{F}$

14. The equivalent capacitance of the circuit shown, between points A and B will be

- 1)  $\frac{2}{3} \mu\text{F}$
- 2)  $\frac{5}{3} \mu\text{F}$
- 3)  $\frac{8}{3} \mu\text{F}$
- 4)  $\frac{7}{3} \mu\text{F}$

15. The value of equivalent capacitance of the combination shown in figure between the points P and G is

- 1)  $3C$
- 2)  $2C$
- 3)  $C$
- 4)  $C/3$

16. The equivalent capacitance between the points a and b in the diagram is

- 1)  $1 \text{ pF}$
- 2)  $1.5 \text{ pF}$
- 3)  $2 \text{ pF}$
- 4)  $2.5 \text{ pF}$