



OHM'S LAW AND KIRCHHOFF'S LAW





MAGNETIC EFFECT OF AN ELECTRIC CURRENT

Vikasana – CET 2012



1

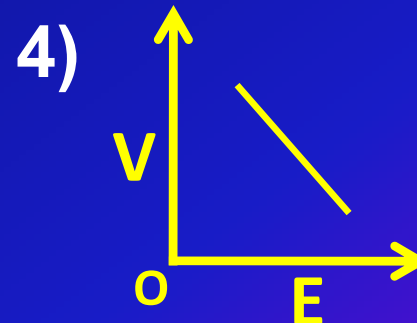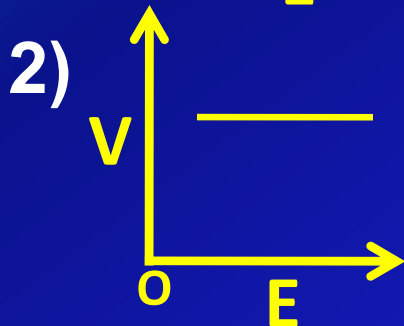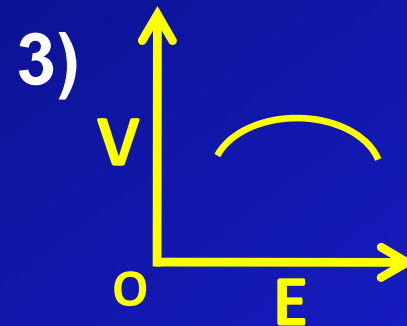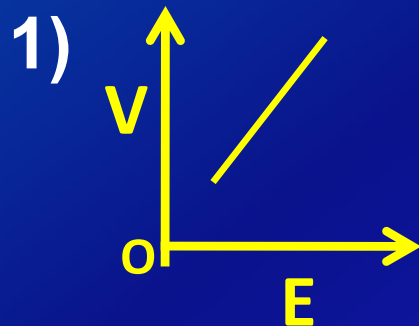A conductor obeys Ohm's law. Which of the following correctly represents the variation of drift velocity ' v ' with applied electric field ' E '?





2

The drift velocity of electrons in a wire of radius 'r' is proportional to

- 1) r
- 2) r^2
- 3) r^3
- 4) none of the above



3

A current of 10A flows through a conductor of resistance 10Ω for 10 minutes. The number of electrons moved is

- 1) 6.25×10^{20}
- 2) 3.75×10^{22}
- 3) 6.25×10^{22}
- 4) 3.75×10^{20}



4

A wire of length 2m is stretched uniformly so that the length becomes 6m. Then its resistance will be

- 1) decreases to $\frac{1}{3}$ of the original value**
- 2) increase to 3 times the original value**
- 3) decreases $\frac{1}{9}$ times the original value**
- 4) increases to 9 times the original value**



5

The resistance of a conductor is 5Ω at 50°C and 6Ω at 100°C . Its resistance at 0°C is

- 1) 4Ω
- 2) 4.5Ω
- 3) 5Ω
- 4) 5.5Ω



6

The colour of the first three rings in a resistor for a resistance of $1.2 \text{ M}\Omega$ is

- 1) brown, orange, green
- 2) brown, red, blue
- 3) brown, red, green
- 4) brown, blue, green



7

A 3°C rise of temperature is observed in a conductor by passing a certain current. When the current is doubled the rise of temperature will be

- 1) 15°C
- 2) 12°C
- 3) 9°C
- 4) 30°C



8

A cell of emf E is connected to a resistance of R , the potential difference between the terminals of the cell is V . Then the internal resistance of the cell must be

1) $\frac{2(E-V)V}{R}$

3) $\frac{(E-V)R}{V}$

2) $\frac{2(E-V)R}{E}$

4) $(E-V)R$



9

The essential requirements of a fuse wire are

- 1) high resistance and high melting point**
- 2) high resistance and low melting point**
- 3) low resistance and low melting point**
- 4) low resistance and high melting point**



10

The variation of resistance R of a thermistor with temperature T is represented by $R = a e^{b/T}$. In the above relations the units of a and b are respectively.


- 1) ohm, per kelvin
- 2) ohm, kelvin
- 3) per ohm, per kelvin
- 4) both have no units



11

The resistance between A and B in the figure is

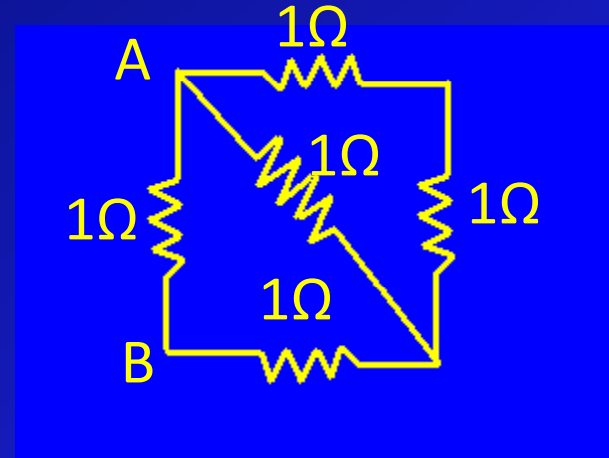- 1) $5/8 \Omega$
- 2) $8/5 \Omega$
- 3) $3/2 \Omega$
- 4) $2/3 \Omega$






12

Find the value of I in the following circuit

- 1) 0.25 A
- 2) 0.5 A
- 3) 1 A
- 4) 2 A

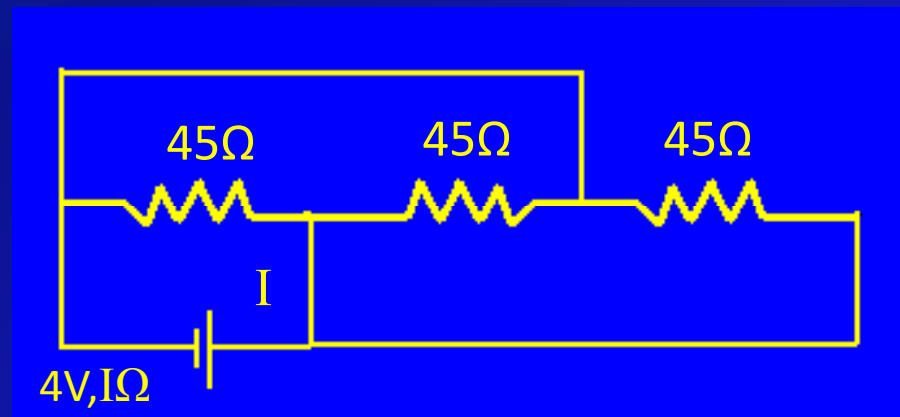



13

How many 400Ω resistors connected in parallel are required to carry a total current of 1.5A on a 150V line?

- 1) 10
- 2) 20
- 3) 4
- 4) 80



14

The effective resistance of two resistors when connected in parallel is 10Ω . If one of the resistors is 20Ω , then the other resistance is


- 1) $10\ \Omega$
- 2) $15\ \Omega$
- 3) $20\ \Omega$
- 4) $100\ \Omega$



15

What is the p.d. across 4Ω ?

- 1) 3.2 V
- 2) 8V
- 3) 4 V
- 4) 2 V

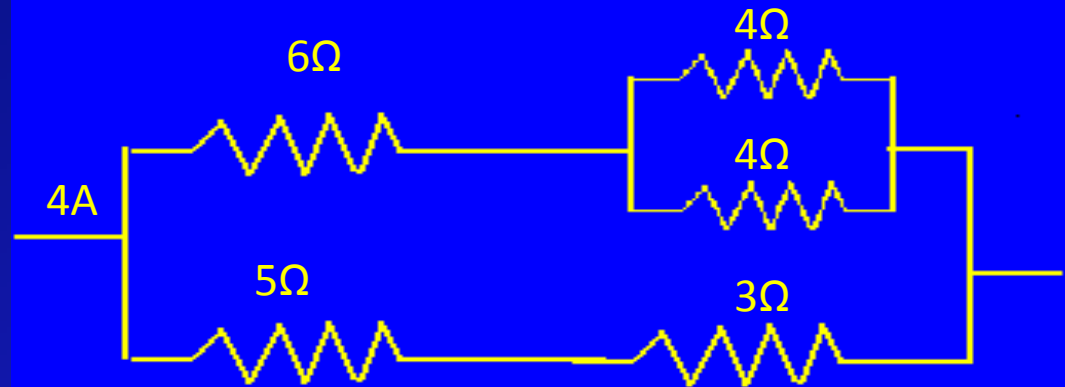



16


In a metre bridge, when the resistances in the two gaps are in the ratio 3 : 5, then the balancing length ' ℓ ' is given by

- 1) 0.475 m
- 2) 0.5 m
- 3) 0.375 m
- 4) 0.675 m

17

In the circuit shown in the figure, the current through two ohm resistor is

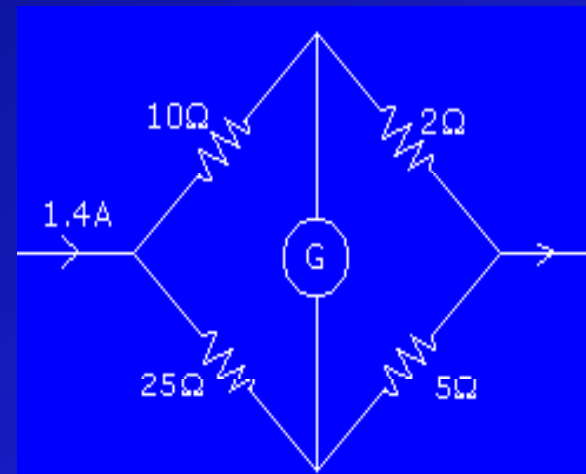- 1) 1.2 A
- 2) 1 A
- 3) 0.8 A
- 4) 0.4 A





18

Four resistances 15, 12, 4 and 10Ω are connected in cyclic order to form Wheatstone network. The resistance to be connected in parallel with 10Ω to balance the network is

- 1) 5Ω
- 2) 10Ω
- 3) 8Ω
- 4) 20Ω



19

Consider the following statements

- i) Kirchhoff's voltage law follows from the law of conservation of energy**
- ii) Kirchhoff's Current law follows from the law of conservation of charge**
- iii) Kirchhoff's voltage law propounds the conservation nature of electric field**

The correct statements are


- | | |
|------------------------|-------------------------|
| 1) i) and ii) | 2) i) and iii) |
| 3) ii) and iii) | 4) all the three |



20

In the diagram $V_A - V_B =$

- 1) 2 V
- 2) 1 V
- 3) 3.5 V
- 4) 1.5 V

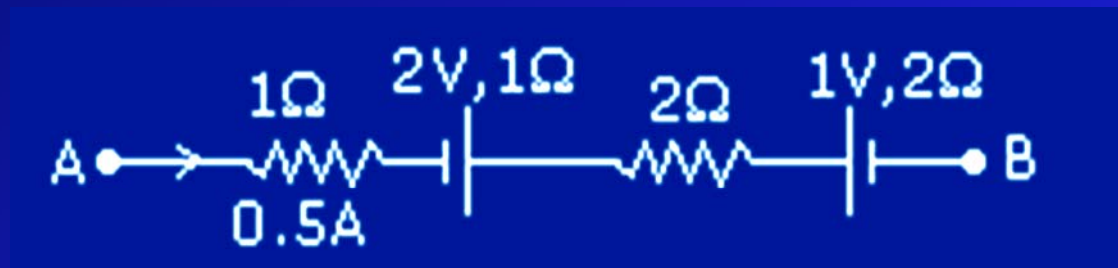



21

When a current flows in a conductor, the order of magnitude of drift velocity of electrons through it is

- 1) 10^{-7} ms^{-1}
- 2) 10^{-5} ms^{-1}
- 3) 10^4 ms^{-1}
- 4) 10 ms^{-1}



22

When a current I is set up in a wire of radius ' r ', the drift speed is ' v_d '. If the same current is set up through a wire of radius ' $2r$ ' the drift speed will be

- 1) $v_d / 4$
- 2) $v_d / 2$
- 3) $2 v_d$
- 4) $4 v_d$



23

If the flash gun of a camera operates for a milli second and during this time 0.05 coulomb of charge flows then the current will be

- 1) 5×10^{-3} A
- 2) 5×10^{-5} A
- 3) 0.02 A
- 4) 50 A



24

Two aluminium wires are of same length, one is twice as thick as the other. The resistances are in the ratio

- 1) 16 : 1
- 2) 8 : 1
- 3) 4 : 1
- 4) 2 : 1



25

The temperature coefficient of resistance of a wire is $0.00125/^\circ\text{C}$. At 0°C its resistance is 1Ω . The resistance of the wire will be 2Ω at

- 1) 800°C
- 2) 1073°C
- 3) 125°C
- 4) 400°C



26

'Ampere second' is the unit of

- 1) Current
- 2) Power
- 3) Charge
- 4) emf



27

A 100 W and 25 W bulb are designed for the same voltage. They have filament of same length and material. The ratio of the diameter of the 100 W bulb to that of the 25W bulb is

- 1) 4 : 1
- 2) 2 : 1
- 3) $\sqrt{2}$: 1
- 4) 1 : 2



28

The resistivity of a wire depends upon its

- 1) length
- 2) mass
- 3) material
- 4) area of cross-section



29

The colour bands in a certain resistor are in the order red-orange-brown. The resistance of the resistor is

- 1) 230Ω
- 2) 2300Ω
- 3) 320Ω
- 4) 32Ω



30

The essential requirements for a good heating element are

- 1) high resistivity and low melting point
- 2) high resistivity and high melting point
- 3) low resistivity and low melting point
- 4) low resistivity and high melting point



31

An electron is moving in a circle of radius 'r' in a uniform magnetic field B. Suddenly the field is reduced to B/2. The radius of the circle now becomes


- 1) $r/2$
- 2) $r/4$
- 3) $2r$
- 4) $4r$

32

A portion of a long straight wire carrying a current I , is bent in the form of a semicircle of radius ' r ' as shown in the figure. The magnetic field at the centre O of the semicircle, in tesla is

- 1) $\frac{\pi I}{2r} \times 10^{-7}$
- 2) $\frac{\pi I}{2r}$
- 3) $\frac{\pi I}{r} \times 10^{-7}$

4) Zero

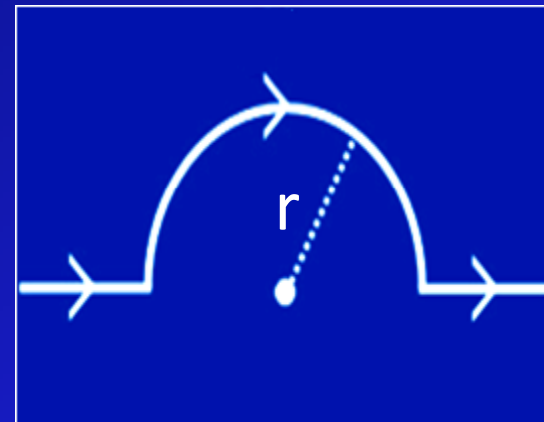

33

A straight conductor carrying a current I , is split into a circular loop of radius ' r ' as shown in the figure. The magnetic field at the centre O of the circle, in tesla is

1) $\frac{\mu_0 I}{\pi r}$

3) $\frac{\mu_0 I}{2r}$

2) $\frac{\mu_0 I}{2\pi r}$

4) Zero





34

A current I flows in a circular arc of wire which subtends an angle $3\pi/2$ at the centre. If the radius of the circle is r , then the magnetic induction B is

1) $\frac{\mu_0 I}{2r}$

3) $\frac{2\mu_0 I}{4r}$

2) $\frac{\mu_0 I}{\pi r}$

4) $\frac{3\mu_0 I}{8r}$



35

A current I flows along infinitely long straight thin conductor, then the magnetic field at any point on the conductor is

1) ∞

2) 0

3) $\frac{\mu_0 I}{4\pi}$

4) $\frac{\mu_0 I}{2\pi}$



36

A circular current carrying coil has a radius R . The distance from the centre of the coil on the axis where B will be $1/8$ of its value at the centre of the coil is

- 1) $r / \sqrt{3}$
- 2) $\sqrt{3} r$
- 3) $2 \sqrt{3} r$
- 4) $2r / \sqrt{3}$



37

A charge 'q' coulomb is circulating in an orbit of radius 'r' metres making 'n' revolutions per second. The magnetic field produced at the centre of the circle in N/Am is

1) $\frac{2\pi q}{nr} \times 10^{-7}$

3) $\frac{2\pi nq}{r} \times 10^{-7}$

2) $\frac{2\pi q}{r} \times 10^{-7}$

4) $\frac{2\pi rn}{q} \times 10^{-7}$



38

Two tangent galvanometers A and B are connected in series a current flowing through them produces deflection of 30° and 60° respectively. The reduction factors of the galvanometers in the ratio

- 1) $\sqrt{3} : 1$
- 2) $1 : \sqrt{3}$
- 3) $3:1$
- 4) $1:3$



39

Two tangent galvanometers A and B have radii in the ratio 2 : 3 and turns in the ratio 1 : 3. When a certain current flows through both of them a deflection of 30° is produced in A. What is the deflection produced in B?


- 1) $\theta = \tan^{-1} (2/\sqrt{3})$
- 2) $\theta = \tan^{-1} (3/2)$
- 3) $\theta = \tan^{-1} (\sqrt{3})$
- 4) $\theta = \tan^{-1} (\sqrt{2})$



40

A long straight conductor carrying a current I ; is bent into the shape shown in the figure. The radius of the circular loop is r . The magnetic field at the centre of the loop is

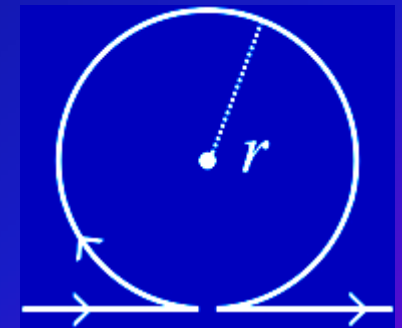1) $\frac{\mu_0 I}{2r} \left(1 - \frac{1}{\pi}\right)$ into the page 3) $\frac{\mu_0 I}{2r} \left(1 - \frac{1}{\pi}\right)$ out of the page



2) $\frac{\mu_0 I}{2r} \left(1 + \frac{1}{\pi}\right)$ out of the page 4) $\frac{\mu_0 I}{2r} \left(1 + \frac{1}{\pi}\right)$ into the page



THANK YOU

Vikasana – CET 2012